
Basmala Moumneh 1006091676 moumnehb

Lab 5:

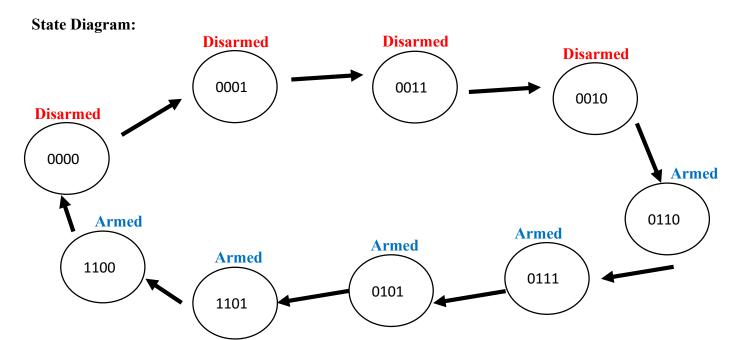

State Table:

F0	F1	F2	F3	F0	F1	F2	F3
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	1
0	0	1	1	0	0	1	0
0	0	1	0	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	0	1	0	1
0	1	0	1	1	1	0	1
1	1	0	1	1	1	0	0
1	1	0	0	0	0	0	0

Basmala Moumneh 1006091676 moumnehb

State Table LED:

F0	F1	F2	F3	LED
0	0	0	0	0
0	0	0	1	0
0	0	1	1	0
0	0	1	0	0
0	1	1	0	1
0	1	1	1	1
0	1	0	1	1
1	1	0	1	1
1	1	0	0	1

K-Maps:

F0:

	F0'F1'	F0'F1	F0F1	F0F1'
F2'F3'	0	X	0	X
F2'F3	0	1	1	X
F2F3	0	0	X	X
F2F3'	0	0	X	X

\rightarrow F0 = F1F2'F3

Basmala Moumneh 1006091676 moumnehb

F1:

	F0'F1'	F0'F1	F0F1	F0F1'
F2'F3'	0	X	0	X
F2'F3	0	1	1	X
F2F3	0	1	X	X
F2F3'	1	1	X	X

$\rightarrow F1 = F2F3' + F3F1$

F2:

	F0'F1'	F0'F1	F0F1	F0F1'
F2'F3'	0	X	0	X
F2'F3	1	0	0	X
F2F3	1	0	X	X
F2F3'	1	1	X	X

$\rightarrow F2 = F1'F3 + F2F3'$

F3:

	F0'F1'	F0'F1	F0F1	F0F1'
F2'F3'	1	X	0	X
F2'F3	1	1	0	X
F2F3	0	1	X	X
F2F3'	0	1	X	X

\rightarrow F3 = F0'F1 + F2'F1' + F2F1

LED:

	F0'F1'	F0'F1	F0F1	F0F1'
F2'F3'	0	X	1	X
F2'F3	0	1	1	X
F2F3	0	1	X	X
F2F3'	0	1	X	X

 \rightarrow LED = F1

Equations:

- F0 = F1F2'F3
- F1 = F2F3' + F3F1
- F2 = F1'F3 + F2F3'
- F3 = F0'F1 + F2'F1' + F2F1
- LED = F1

Screen Shot Of Circuit Diagram When The Output LED Just Became "Armed":

